

Contents

Preface, ix

1	Mechanical System Interfacing: Introduction	1
1.1	The Interface	2
1.2	Mechanical System Design Philosophy	2
1.3	Mechanical System Time Scales	4
1.4	Major Topics	5
1.5	Problems and Discussion Topics	5
2.	Combinational Digital Logic	7
2.1	Quantized Signals	7
2.2	Error-Free Coding	8
2.3	Static/Dynamic, Algebra/Calculus	9
2.4	Counting and Binary Numbers	9
2.5	Gray Code	10
2.6	Boolean Algebra	11
2.7	Boolean Equations	12
2.8	Axioms	13
2.9	Theorems	13
2.10	Logic System Design	13
2.10.1	Function Generation from Truth Tables	14
2.11	Logic Function Minimization	15
2.12	Karnaugh Map	17
2.13	Don't Care Combinations	18
2.14	Hazards	18
2.15	Physical Realization of Boolean Functions	20
2.15.1	Relay Logic	20
2.15.2	Programmable Logic Controllers (PLC)	21
2.15.3	Implementation Conventions	21
2.15.4	Fluid Logic	21
2.15.5	Electronic Logic	21

2.15.6 Logic Block Diagrams	22
2.15.7 Door Latch in Circuit Form	23
2.15.8 Practical Considerations	23
2.15.9 Connecting to a Bus	25
2.15.10 Analog-Digital Conversion: The Schmidt Trigger	25
2.16 Programmable Logic Devices	26
2.16.1 ROM as a Logic Device	27
2.16.2 PAL, Programmable AND, Fixed OR; PLA, Both Programmable	28
2.16.3 Erasable PLDs	30
2.16.4 Logic Optimizing Compiler (LOC) Input	31
2.17 Problems and Discussion Topics	34
3 Synchronous Sequential Logic	37
3.1 Flip-Flops	38
3.2 Synchronous Systems	43
3.3 State Transition Logic	44
3.4 Next-State Table	44
3.5 State Assignment	45
3.6 Memory Elements for Synchronous Circuits: D Flip-Flops	45
3.7 Other Synchronous Memory Elements	48
3.8 Using EPLDs for State Machines	49
3.9 Asynchronous Inputs	53
3.10 Moore-Mealy Machines	54
3.11 State Table Reduction	54
3.12 Metastability	55
3.13 Problems and Discussion Topics	56
4 Asynchronous Sequential Logic	59
4.1 Flow Tables	59
4.1.1 Set-Reset Flip-Flop Design	60
4.1.2 Flow Table Reduction	61
4.1.3 State Assignment	61
4.1.4 Excitation Map	62
4.2 Hazards	63
4.3 Design of a Toggle Flip-Flop	63
4.4 State Adjacency	65
4.5 Output Assignment	67
4.6 Excitation Network	68
4.7 Asynchronous Design for Door Lock	68
4.8 PLDs and Asynchronous Logic	69
4.9 Problems and Discussion Topics	69
5 Simple Computer Structure: Register Transfer Logic	73
5.1 Registers	74
5.2 Data Bus	74

5.3	Control Signals	76
5.4	Input–Output Bus	77
5.5	Commercially Available Buses	78
5.6	Multiple Processor Buses	79
5.7	Problems and Discussion Topics	79
6	Embedded Control Computers	81
6.1	Motivation, Application Requirements, and Architectures	82
6.2	Basic Features of Embedded Computers	83
6.2.1	Memory	83
6.3	Architectures of Single-Chip Computers: Microcontrollers	84
6.3.1	Basic Architecture	84
6.3.2	Architectural Evolution	85
6.3.3	On-Chip Input–Output	86
6.3.4	High-Speed Input–Output	87
6.3.5	Microcontroller Configurations	87
6.4	Digital Signal Processors	88
6.5	RISC and High-Speed Floating Point	89
6.6	Embedded Application of PCs	90
6.7	Watchdog Timers	90
6.8	Software Development Environment	91
6.8.1	Example 1: Consumer Product, four-bit Processor	92
6.8.2	Example 2: Technologically Complex Control Application	92
6.8.3	Computationally Intensive Signal Processing or Control	93
6.8.4	Example 4: Application with Data Base or Archival Needs	94
6.9	Problems and Discussion Topics	94
7	Stepping Motors	97
7.1	Permanent Magnet Stepping Motors	98
7.2	Stepping Sequence	98
7.3	Excitation Sequence	99
7.4	Physical Configuration	100
7.5	Pulse Excitation	100
7.6	Variable Reluctance Stepping Motors	101
7.7	Stepping Motor Performance	102
7.7.1	Resonance	102
7.7.2	Static Operation	103
7.7.3	Dynamic Behavior	103
7.8	Thermal Characteristics	105
7.9	Software Stepping Motor Control	105
7.10	Fractional Stepping	107
7.10.1	Half Stepping	107
7.10.2	Microstepping	108
7.11	Torque Characteristics	110

7.12 Problems and Discussion Topics	111
8 DC Motors	113
8.1 Coil-Field Interaction	113
8.2 Commutation	114
8.3 Operating Characteristics	116
8.4 Motor-Driven System	117
8.5 Generators/Tachometers	118
8.6 Brush Problems	119
8.7 DC Motor Types	119
8.7.1 Field-Wound Motors	119
8.7.2 Permanent Magnet Motors	119
8.7.3 Ironless Core Motors	120
8.7.4 Linear Motors	120
8.8 Impedance Matching	121
8.8.1 Optimum Gear Ratio	122
8.9 Thermal Characteristics	123
8.10 Motor Control	124
8.10.1 Voltage Control	124
8.10.2 Torque-Current Control	124
8.10.3 Velocity Control	125
8.10.4 Dynamic Compensation	127
8.10.5 Position Control	128
8.11 Brushless Motors	132
8.11.1 Brushless Motor Configuration	133
8.11.2 Pros and Cons of Brushless Motors	133
8.12 Computer Interface Requirements	134
8.12.1 Supervisory Control	134
8.12.2 Direct Digital Control	135
8.12.3 Instrument and Actuation Interfaces	135
8.13 Problems and Discussion Topics	136
9 Analog ↔ Digital Conversion	139
9.1 Coding	140
9.2 Digital-to-Analog Conversion	143
9.3 Flash Analog-to-Digital Conversion	144
9.4 Successive-Approximation A/D	146
9.5 Integrating Converters	148
9.6 Sigma-Delta One-Bit Converters	149
9.6.1 Delta Modulation	149
9.6.2 Sigma-Delta Modulation	150
9.6.3 Sigma-Delta Analog-to-Digital Converter	152
9.6.4 Sigma-Delta Digital-to-Analog Converters	155
9.6.5 Sigma-Delta Design Considerations	156
9.7 Sampling	156

9.7.1 Aliasing	156
9.7.2 Oversampling	158
9.8 Problems and Discussion Topics	159
10 Position and Velocity Measurement	161
10.1 Analog/Digital: Precision, Range, and Accuracy	162
10.1.1 Analog Velocity Measurement	163
10.1.2 Noise and Precision	163
10.1.3 Range	164
10.1.4 Velocity Control	164
10.2 Pulse Measurement of Velocity	167
10.2.1 Pulse Generation Devices	167
10.2.2 Frequency-to-Voltage Converters	168
10.2.3 Logic Measurement of Frequency	168
10.2.4 Software Measurement of Frequency	169
10.2.5 Precision in Pulse Measurement of Frequency	169
10.2.6 Period Measurement	170
10.3 Analog Position Measurement	171
10.4 Incremental Encoders	173
10.4.1 Quadrature	173
10.4.2 Reliability	175
10.4.3 Decoding Technologies	175
10.4.4 Optical Shutter	177
10.4.5 Microdecoding	177
10.4.6 Velocity From Encoders	178
10.4.7 Linear and Rotary Encoders	178
10.5 Laser Interferometry	179
10.6 Synchros and Resolvers	180
10.6.1 Inductive Coupling	180
10.6.2 Input-Output Relationships	181
10.6.3 Conversion to Position and Velocity Signals	182
10.6.4 Velocity	186
10.6.5 Resolver-to-Digital Converters	186
10.6.6 Rotary/Linear Conversion, Multistage	187
10.7 Absolute Encoders	187
10.8 Problems and Discussion Topics	190
11 Operational Amplifiers for Analog Signal Processing	193
11.1 The High-Gain DC Amplifier	194
11.2 Computing Functions Using Inverting Amplifier	196
11.2.1 Static Linear Functions	196
11.2.2 Dynamic Linear Functions	196
11.2.3 Analog Computers	198
11.2.4 Nonlinear Functions	200
11.2.5 Comparator	203

11.3 Follower Configurations	204
11.4 Digital-to-Analog Converters	206
11.5 Functional Characteristics	208
11.5.1 741 Op-Amp	209
11.5.2 Open-Loop Gain	209
11.5.3 Input Impedance	209
11.5.4 Output Impedance	210
11.5.5 Input Offset Voltage	210
11.5.6 Bandwidth	210
11.6 Problems and Discussion Topics	210
12 Power Amplifiers	213
12.1 Introduction	213
12.1.1 Overview	213
12.1.2 Voltage Output vs. Current Output	214
12.1.3 Linear vs. PWM Amplifiers	216
12.2 Power Transistors	218
12.2.1 Background	218
12.2.2 Bipolar Transistors	219
12.2.3 MOSFET Transistors	222
12.3 Linear Amplifiers	223
12.3.1 Class B Output Stage	223
12.3.2 Reducing Crossover Distortion	225
12.3.3 Using Feedback within the Amplifier	225
12.3.4 Thermal Stability	227
12.3.5 Variations on the Class A-B Output	228
12.4 PWM Amplifiers	229
12.4.1 Basic Operation	229
12.4.2 PWM Input From an Analog Source	229
12.4.3 PWM Input From a Digital Source	231
12.4.4 Signal Conditioning	231
12.5 Power Op-Amps	233
12.5.1 Overview	233
12.5.2 Advantages and Disadvantages	233
12.5.3 Application Hints	233
12.6 Adding Robustness and Troubleshooting	233
12.6.1 Power Supply Considerations	233
12.6.2 Thermal Considerations	234
12.7 Problems and Discussion Topics	235
Bibliography	237
Index	239