Contents

The numbers in parentheses after each section name identify the previous sections that constitute the minimum prerequisite material. The symbol † identifies optional material that may be omitted without loss of continuity.

Chapter 1 Introduction 1

1.1 The Scope of Electrical Engineering *1*
1.2 Historical Perspective *3*
1.3 Prospectus *5*

Part I Linear Circuits

Chapter 2 Circuit Concepts 9

2.1 Current, Voltage, and Power *10*
Charge and Current *Energy and Voltage* *Electric Power* *Magnitude Prefixes*

2.2 Sources and Loads (2.1) *15*
i-v Curves *Ideal Sources* *Devices and Models* *Controlled Sources*

2.3 Resistance (2.2) *22*
Ohm's Law *Power Dissipation and Ohmic Heating* *Conduction and Resistivity* *Lumped Parameter Circuits*

2.4 Kirchhoff's Laws (2.3) *30*
Kirchhoff's Current Law *Kirchhoff's Voltage Law* *Series and Parallel Circuits* *Branch Currents and Node Voltages*

Problems *41*

Chapter 3 45

3.1 Series and Parallel Resistance (2.4) *46*
Series Resistance and Potentiometers *Parallel Resistance* *Series/Parallel Reduction* *Source Loading and Power Transfer*

3.2 Circuit Theorems (3.1) *56*
Equivalence and Equivalent Resistance *Thévenin's Theorem* *Superposition*

3.3 Node and Loop Analysis† (3.2) *66*
Node Analysis Loop Analysis Circuits with Controlled Sources

3.4 DC Meters and Measurements† (3.2) *76*
Voltmeters and Ammeters Ohmmeters
Bridges and Null Measurements

Problems *82*

Chapter 4 Amplifiers and Op-Amps 87

4.1 Amplifier Concepts (3.2) *88*
Ideal Amplifiers Amplifier Models and Analysis
Power Gain and Decibels Cascaded Amplifiers

4.2 Operational Amplifiers (4.1) *97*
Op-amp Characteristics Noninverting Amplifiers
Inverting and Summing Amplifiers
Input and Output Resistance†

Problems *108*

Chapter 5 Capacitance, Inductance, and Impedance 113

5.1 Capacitance and Inductance (3.3) *114*
Capacitors and Capacitance Inductors and Inductance
DC Steady-State Behavior
Equivalent Inductance and Capacitance

5.2 Dynamic Circuits (5.1) *124*
Differential Circuit Equations
Natural Response
Forced and Complete Response

5.3 Impedance and Transfer Functions (5.2) *133*
The Impedance Concept
Circuit Analysis Using Impedance and Admittance
Transfer Functions

Problems *144*

Chapter 6 AC Circuits 149

6.1 Sinusoids and Phasors (5.3) *150*
Sinusoidal Waveforms Phasor Representation Complex Algebra

6.2 AC Impedance (6.1) *157*
AC Impedance and Admittance AC Resistance and Reactance
Impedance Calculations

6.3 AC Circuit Analysis (6.2) *164*
Phasor Diagrams Resonance Instantaneous and Average Power
AC Superposition†

6.4 Transformer Circuits (6.3) *178*
The Ideal Transformer Impedance Reflection
Maximum Power Transfer†

6.5 Residential Circuits and Wiring† (6.1) *186*
Dual-Voltage Service Entrance Wiring and Grounding

Problems *191*

Chapter 7 Frequency Response and Transients 197

7.1 Frequency Response and Filters (6.2) *198*
Lowpass and Highpass Filters *Bandpass Filters*
Op-amp filters†

7.2 Bode Plots† (7.1) *211*
Factored Transfer Functions *First-Order Functions*
Second-Order Functions

7.3 First-Order Transients (7.1) *218*
Natural Response of RC *and* RL *Circuits*
Switched DC Transients
Step and Pulse Response

7.4 Second-Order Transients† (7.3) *229*
Overdamped Natural Response *Underdamped Natural Response*
Critical Damping *Complete Response*

Problems *239*

Part II Electronic Devices and Circuits

Chapter 8 Diodes and Semiconductors 249

8.1 Ideal and Semiconductor Diodes (3.2) *250*
The Ideal Diode *Semiconductor Diodes*
Semiconductors and Doping pn *Junctions*

8.2 Diode Circuit Analysis (8.1) *261*
Load-Line Analysis *Forward-Bias Models*
Reverse Breakdown and Zener Diodes *Breakpoint Analysis*

8.3 Special-Purpose Devices† (5.1 and 8.1) *272*
Junction Capacitance and Varactors
Ohmic Contacts and Schottky Diodes
Photo Devices *Thermistors and Varistors*

Problems *277*

Chapter 9 Transistors and Integrated Circuits 281

9.1 Enhancement MOSFETs (8.3) *282*
Structure and Operation *Static Characteristics*
Universal Curves p-*Channel MOSFETs*

9.2 Depletion MOSFETs and JFETs (9.1) *295*
Depletion MOSFETs *Junction FETs* *Universal Curves*

9.3 Bipolar Junction Transistors (9.1) *301*
Structure and Characteristics *Large-Signal Models*
The pnp *BJT*

9.4 Device Fabrication and Integrated Circuits† (9.3) *311*
Device Fabrication Methods *Planar Processing* *Integrated Circuits*

Problems *319*

Chapter 10 Nonlinear Electronic Circuits 325

10.1 Diode Switching Circuits (7.3 and 8.3) *326*
Clippers and Waveshapers *Digital and Analog Gates*
Peak Detectors and Clamps

10.2 Transistor Switching Circuits (9.3 and 10.1) *336*
BJT Switches and Gates *FET Switches and Gates*
Bistable Flip-Flops *Switching Transients†*

10.3 Trigger and Timing Circuits (4.3 and 10.2) *350*
Comparators and Triggers *Timers and Monostables*
Astable Waveform Generators *The 555 Timer†*

Problems *362*

Chapter 11 Transistor Amplifiers 369

11.1 Small-Signal FET Amplifiers (4.1 and 9.1) *370*
Small-Signal Operation *Common-Source Amplifiers*
Biasing and Design Considerations
Depletion MOSFET and JFET Amplifiers

11.2 Small-Signal BJT Amplifiers (9.3 and 11.1) *382*
Small-Signal BJT Models *Common-Emitter Amplifiers*
Biasing and Design Considerations

11.3 Amplifiers with Feedback (11.2) *391*
Negative Feedback *Feedback Amplifier Circuits*
Voltage Follower Circuits *Multistage Amplifiers*

11.4 Amplifier Frequency Response (7.2 and 11.3) *403*
Frequency-Response Characteristics *Low-Frequency Response*
High-Frequency Response†

11.5 Differential Amplifiers and Op-Amps† (11.3) *412*
Differential Amplification *Integrated-Circuit Op-Amps*

Problems *421*

Chapter 12 Power Electronics 427

12.1 Power Amplifiers (11.3) *428*
Large-Signal Amplification *Transformer-Coupled Amplifiers*
Push-Pull Amplifiers

12.2 Rectifiers and Power Supplies (7.3 and 9.3) *441*
Rectification and Voltage Smoothing *Voltage Regulators*
DC Motor Supplies *Controlled Rectifiers†*

12.3 Thermal Limitations† (9.3) *454*
Thermal Ratings and Derating *Heat Sinks*

Problems *458*

Part III Information Systems

Chapter 13 Signal Processing and Communication Systems 465

13.1 Signals and Spectral Analysis (7.1) *466*
Signal-Processing Systems Periodic Signals and Fourier Series Spectral Analysis and Signal Bandwidth Filtering, Distortion, and Equalization

13.2 Modulation, Sampling, and Multiplexing (13.1) *480*
Frequency Translation and Product Modulation Sampling and Pulse Modulation Multiplexing Systems

13.3 Interference and Noise† (13.2) *488*
Interference, Shielding, and Grounding Electrical Noise Signals in Noise

13.4 Communication Systems† (13.2) *499*
Transmission Lines Radio Transmission Amplitude Modulation Superheterodyne Receivers Frequency Modulation

Problems *512*

Chapter 14 Digital Logic 517

14.1 Digital Logic Concepts (10.2) *518*
Logic Variables and Gates Binary and Decimal Numbers BCD Codes

14.2 Combinational Logic (14.1) *527*
Boolean Algebra Logic Network Design NAND and NOR Logic Minimization with Karnaugh Maps†

14.3 Standard Logic Modules (14.2) *540*
Exclusive-OR Gates Decoders and Demultiplexers Multiplexers Read-Only Memories

14.4 IC Logic Gates and Families† (14.3) *548*
Properties of IC Logic Gates Logic Families IC Gate Circuits

Problems *562*

Chapter 15 Digital Systems 567

15.1 Flip-Flops, Counters, and Registers (14.3) *568*
Latches and Flip-Flops Counters Registers

15.2 Digital Instrumentation (15.1) *585*
Digital-to-Analog Conversion Analog-to-Digital Conversion Data Acquisition and Digital Processing

15.3 Arithmetic Networks (15.1) *598*
Binary Addition Signed Numbers and Subtraction Arithmetic Logic Units Binary Multiplication

15.4 Computers and Microprocessors† (15.3) *607*
Computer Concepts Microprocessors Memory Units

Problems *619*

Part IV Energy Systems

Chapter 16 AC Power Systems 627

16.1 AC Power (6.3) *628*
Real and Reactive Power Apparent Power and Power Factor Wattmeters

16.2 Three-Phase Systems (16.1) *637*
Three-Phase Sources and Symmetrical Sets Balanced Loads Power Measurement Unbalanced Loads†

16.3 Power Transmission and Distribution† (16.2) *650*
Power Transmission Lines Power Networks

Problems *657*

Chapter 17 Magnetics, Induction, and Electromechanics 661

17.1 Magnetics and Induction (5.1) *662*
Magnetic Field and Flux Faraday's Law of Induction Inductance and Stored Energy

17.2 Magnetic Circuits and Materials (17.1) *669*
Magnetic Circuits Magnetization and Hysteresis Losses

17.3 Mutual Inductance and Power Transformers (6.4, 16.1 and 17.2) *677*
Magnetic Coupling and Mutual Inductance Circuit Analysis with Mutual Inductance Power Transformers†

17.4 Electromechanical Transducers (7.3 and 17.2) *689*
Magnetic Force and Induced Voltage Translating-Coil Devices Rotating-Coil Devices Moving-Iron Devices†

Problems *703*

Chapter 18 Rotating Machines 709

18.1 Rotating-Machine Concepts (17.4) *710*
An Elementary Machine Rotating Fields and Poles Machine Performance Characteristics

18.2 Synchronous Machines (16.2 and 18.1) *721*
Three-Phase Generators Three-Phase Fields Synchronous Motors and Capacitors

18.3 AC Motors (18.2) *729*
Three-Phase Induction Motors Starting and Speed Control Single-Phase Induction Motors Special Purpose AC Motors

18.4 DC Machines (18.1) *739*
Commutation and Structural Features Induced EMF and DC Generators DC Motors and the Universal Motor

Problems *750*

Supplementary Reading 755

Cramer's Rule 758

Tables of Mathematical Relations 761

Standard Component Values 763

Answers to Exercises 765

Index 771