

---

# Contents

## CHAPTER I

### Magnetic Systems

1.1	Magnetic Field Concepts	2
1.2	Equivalent Magnetic and Electric Circuits	5
1.3	Energy in a Magnetic Field	8
1.4	Ferromagnetism	9
1.5	Magnetization	12
1.6	Hysteresis	17
1.7	Hysteresis Loss	23
1.8	Eddy Current Loss	25
1.9	Core Losses	29
1.10	Alternating Excitation	31
1.11	Production of Magnetic Flux in Air Gap	34
1.12	Modeling of Magnetic Systems	40

## CHAPTER 2

51

### Transformers

2.1	Ideal Transformers	51
2.1.1	Transformation of Electric Circuit Elements	54
2.2	Equivalent Circuit of a Transformer	56
2.2.1	Winding Resistances	56
2.2.2	Magnetizing Inductance	56
2.2.3	Core Losses	58
2.2.4	Leakage Inductance	59
2.3	Transformer Rating	65
2.3.1	Per Unit Values	66
2.4	Measurement of Transformer Parameters	69
2.5	Transformer Performance	71

**CHAPTER 3****83****Basic Principles of Electric Machines**

3.1 Forces on Electric Currents	84
3.2 Forces on Ferromagnetic Material	86
3.3 Elementary Rotating Machine	88
3.4 Placing Conductors in Slots	93
3.5 Some Elementary Types of Electric Machines	95
3.6 Ferromagnetic Actuator	107
3.7 Reluctance Machines	113

**CHAPTER 4****135****Commutator Machines**

4.1 Magnetic System	135
4.2 Rotor Windings and Commutator	138
4.3 Torque and Generated Voltage	140
4.4 Equivalent Circuit	144
4.5 Steady-State Performance	148
4.6 Motors Operating on Constant Voltage Supply	154
4.7 Operation as a Generator	160

**CHAPTER 5****171****Induction Machines**

5.1 Sinusoidally Distributed Windings	172
5.2 Rotating Magnetic Field	177
5.3 Flux Linkage and Magnetizing Inductance	181
5.4 Torque Production with Squirrel Cage Rotor	185
5.5 Equivalent Circuit Near Synchronous Speed	190
5.6 Machines with Multiple Pole Pairs	193
5.7 Leakage Inductance and Maximum Torque	196
5.8 Rotor Design for Starting Torque	204
5.9 Single-Phase Induction Motors	206

**CHAPTER 6****213****Synchronous Machines**

6.1 Cylindrical Wound-Field Machines	214
6.2 Steady-State Equivalent Circuit	216

6.3	Steady-State Operation	217
6.4	Starting and Excitation of Synchronous Machines	225
6.5	Measurement of Parameters	226
6.6	Permanent Magnet Synchronous Machines	229
6.7	Electrically Switched Permanent Magnet Motors	233

---

**CHAPTER 7** **241****Magnetic Systems and Transformers—Revisited**

7.1	Analysis of Complex Magnetic Systems	241
7.1.1	Equivalent Circuits	242
7.1.2	Equivalent Circuit for a Two-Winding Shell-Type Transformer	250
7.1.3	Synthesis of Magnetic Devices	252
7.1.4	Determination of Leakage Inductance from Dimensions	252
7.2	Design of Inductors and Transformers	255
7.2.1	Heat Transfer	256
7.2.2	Inductor Design	258
7.2.3	Transformer Design	261
7.3	Design of Permanent-Magnet Devices	264
7.4	Variable Frequency Operation of Transformers	268
7.5	Transient Inrush Current of a Transformer	272
7.6	Transformers for Polyphase Systems	274
7.6.1	Connections of Transformers for Three-Phase Systems	274
7.6.2	Polyphase Transformers	279
7.7	Some Special Transformation Devices	282
7.7.1	Autotransformers	282
7.7.2	Instrument Transformers	285
7.8	Forces in Saturable Magnetic Devices	286

---

**CHAPTER 8** **307****Power Semiconductor Converters**

8.1	Power Switching Devices	308
8.2	Controlled Rectifier Systems	310
8.2.1	Single-Phase Controlled Rectifier	311
8.2.2	Three-Phase Controlled Rectifier	317
8.3	Choppers	322
8.3.1	Step-Down Choppers	323
8.3.2	Step-Up Choppers	327
8.3.3	Two- and Four-Quadrant Choppers	329

<b>8.4</b>	Inverters	331
<b>8.4.1</b>	A Simple Voltage-Source Inverter	332
<b>8.4.2</b>	Pulse-Width-Modulated Voltage-Source Inverters	336
<b>8.4.3</b>	Current-Source Inverters	338
<b>8.5</b>	Cycloconverters	342

---

**CHAPTER 9** **347****Commutator Motor Drives**

<b>9.1</b>	Mechanical System Modeling	349
<b>9.2</b>	Dynamic Relations for Drive Systems	354
<b>9.3</b>	Closed-Loop Speed Control	360
<b>9.4</b>	Position Control	365
<b>9.5</b>	Chopper Drives	367
<b>9.6</b>	Controlled Rectifier Drives	372
<b>9.7</b>	Series Commutator Motors	376
<b>9.8</b>	Armature Reaction and Commutation	379

---

**CHAPTER 10** **393****Induction Motor Drives**

<b>10.1</b>	A Transient Model of the Induction Machine	394
<b>10.1.1</b>	An Alternate Form of Transient Model	402
<b>10.1.2</b>	Instantaneous Power and Torque Relations	404
<b>10.1.3</b>	Steady-State Analysis	409
<b>10.1.4</b>	Modeling of Saturation Effects	412
<b>10.1.5</b>	Modeling of Deep Rotor Bar Effects	415
<b>10.2</b>	Variable-Voltage, Variable-Frequency Operation	416
<b>10.2.1</b>	Fundamental-Frequency Performance	416
<b>10.2.2</b>	Effects of Voltage Harmonics	422
<b>10.2.3</b>	Closed-Loop Speed Control	426
<b>10.3</b>	Variable-Current, Variable-Frequency Operation	426
<b>10.4</b>	Variable-Voltage, Constant-Frequency Operation	432
<b>10.5</b>	Speed Control by Rotor-Power Recovery	435
<b>10.6</b>	Unbalanced Operation	438
<b>10.6.1</b>	Operation with One Phase Open	443
<b>10.7</b>	Practical Windings and Space Harmonics	445
<b>10.8</b>	Linear Induction Motors	449

**CHAPTER 11****463****Synchronous Generators, Motors, and Drives**

<b>11.1</b>	<b>Modeling of Synchronous Machines</b>	<b>464</b>
<b>11.1.1</b>	<b>Cylindrical-Rotor Machines</b>	<b>464</b>
<b>11.1.2</b>	<b>Representation of Magnetic Saturation</b>	<b>472</b>
<b>11.1.3</b>	<b>Modeling of Saliency</b>	<b>473</b>
<b>11.1.4</b>	<b>Measurement of Parameters</b>	<b>485</b>
<b>11.2</b>	<b>Electrical Transient Performance</b>	<b>487</b>
<b>11.3</b>	<b>Electromechanical Transient Performance</b>	<b>496</b>
<b>11.4</b>	<b>Permanent-Magnet Synchronous Motors</b>	<b>503</b>
<b>11.4.1</b>	<b>Machines with Surface-Mounted Magnets</b>	<b>503</b>
<b>11.4.2</b>	<b>Machines with Inset Magnets</b>	<b>508</b>
<b>11.4.3</b>	<b>Machines with Circumferential Magnets</b>	<b>510</b>
<b>11.4.4</b>	<b>Hysteresis Motors</b>	<b>511</b>
<b>11.5</b>	<b>Variable-Frequency Synchronous Motor Drives</b>	<b>512</b>
<b>11.5.1</b>	<b>Open-Loop Drive Systems</b>	<b>513</b>
<b>11.5.2</b>	<b>Self-Controlled Drive Systems</b>	<b>516</b>
<b>11.6</b>	<b>Switched Reluctance Motor Drives</b>	<b>520</b>
<b>11.7</b>	<b>Stepper Motor Drives</b>	<b>524</b>

---

**Appendices**

<b>A</b>	<b>SI Unit Equivalents</b>	<b>539</b>
<b>B</b>	<b>Physical Constants</b>	<b>541</b>
<b>C</b>	<b>Resistivity and Temperature Coefficient of Resistivity of Some Conductive Materials</b>	<b>542</b>
<b>D</b>	<b>Wire Table</b>	<b>543</b>

**Answers to Problems****545****Index****549**